

Ohm's Law & Kirchhoff's Laws

Resistance - measure of how easily current flows.


- scalar - symbol = R - units = Ohms (Ω)
- depends on length, cross-sectional area, material
 - long, thin wires $\rightarrow$ more resistance.
- Converts electrical energy into thermal energy
 - $\rightarrow$ Good - lightbulb, stove, hair dryer
 - $\rightarrow$ Bad - xBox 360, computer

Resistors have resistance

- wires + batteries do, but we'll ignore that.

Equivalent Resistance - total resistance of several resistors.


Series

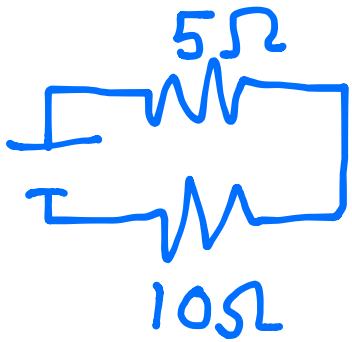

$$R_{eq} = 15\Omega$$

$$R_{eq} = R_1 + R_2 + \dots + R_N$$

Parallel

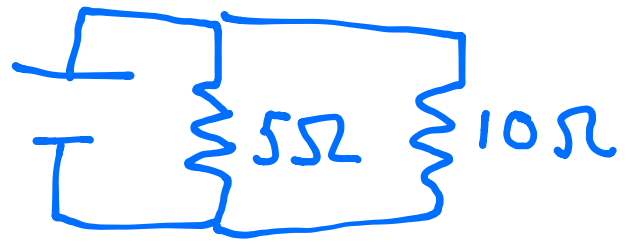

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}}$$

$$\begin{aligned} R_{eq} &= \frac{1}{\frac{1}{5} + \frac{1}{10}} = \frac{1}{\frac{2}{10} + \frac{1}{10}} \\ &= \frac{1}{3/10} \\ &= 3.33\Omega \end{aligned}$$


Ohm's Law - relates
voltage, current, and resistance

$$V = IR \quad I = V/R \quad R = \frac{V}{I}$$

A toaster is connected to 110V
and 2A runs through it.

$$R = \frac{110}{2} = 55\Omega$$

Circuits are like water slides:

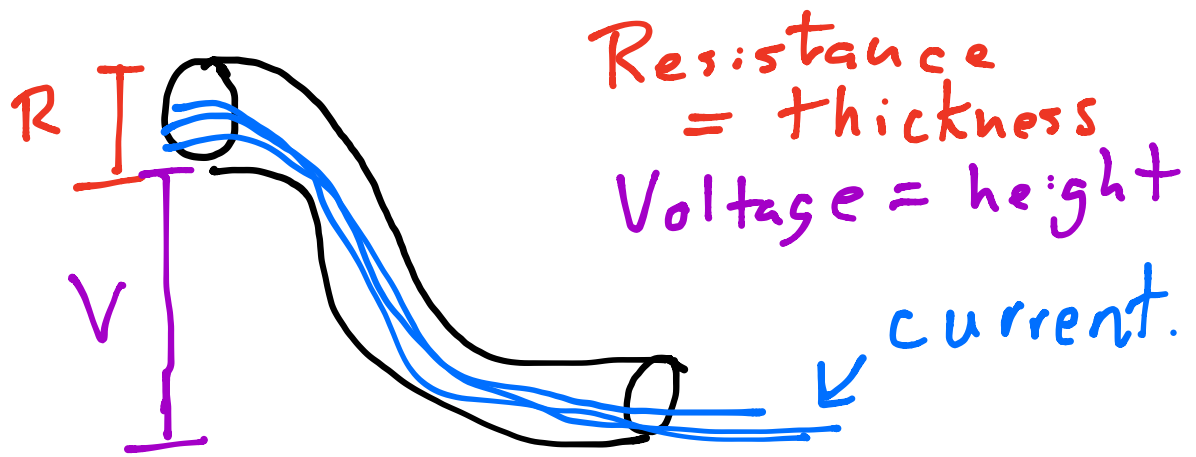

Joule's Law - power in circuits

$$P = W/t \quad W = Vq$$

↓

$$P = \frac{Vq}{t} \Rightarrow P = IV$$

$$P = IV = I(IV) = I^2 R$$

↪ Joules Law

$$P = IV = \left(\frac{V}{R}\right)V = \frac{V^2}{R}$$

↪ Joule again

The toaster's power is:

$$P = IV = 2 \cdot 110 = 220 \text{ W}$$

or

$$P = I^2 R = 2^2 \cdot 55 = 220 \text{ W}$$

$$P = \frac{V^2}{R} = \text{or } \frac{110^2}{55} = \frac{12100}{55} = 220 \text{ W}$$

Kirchoff's Laws

1. Law of Currents

- the total current entering a junction = current leaving the junction.

2. Law of Voltages

- the total voltage drop around a path of a circuit = voltage of the battery

